



**Figure 1** Optocoupler IC<sub>1</sub> isolates the control circuit's input and output.